 


PHYS 220 Physical Electronics Problem Set #5 SOLUTIONS

It+It 4.2, 4.3, additional exercise #2

8.5, 8.7, 8.8, 8.9

4.2 The Howland Current Source



Since the op-amp keeps its inputs at the same potential, the voltage across R_4 equals the voltage across R_3

$$-I_3 R_3 = I_1 R_4 \quad (1)$$

↑ to be consistent with directions shown on diagram

Since no current flows into or out of the op-amp inputs (and charge is conserved)

$$I_3 = I_2 + I_{load} \quad (2)$$

Putting (2) into (1) $\Rightarrow I_2 R_3 + I_{load} R_3 = -I_1 R_4$

or...
$$I_{load} = -I_1 \left(\frac{R_4}{R_3} \right) - I_2$$

Now $I_2 = \frac{V_+}{R_2} = \frac{V_-}{R_2}$ since $V_+ = V_-$

and... $V_- = V_{in} - I_1 R_1$, so...

$$I_{load} = -I_1 \left(\frac{R_4}{R_3} \right) - \frac{V_{in}}{R_2} + I_1 \frac{R_1}{R_2}$$


or... $I_{load} = -\frac{V_{in}}{R_2} + I_1 \left[\frac{R_1}{R_2} - \frac{R_4}{R_3} \right]$
 set this to zero...

choosing $\frac{R_1}{R_2} = \frac{R_4}{R_3}$ or $\frac{R_3}{R_2} = \frac{R_4}{R_1}$, then


$$I_{load} = -\frac{V_{in}}{R_2}$$

 as indicated on p. 182.

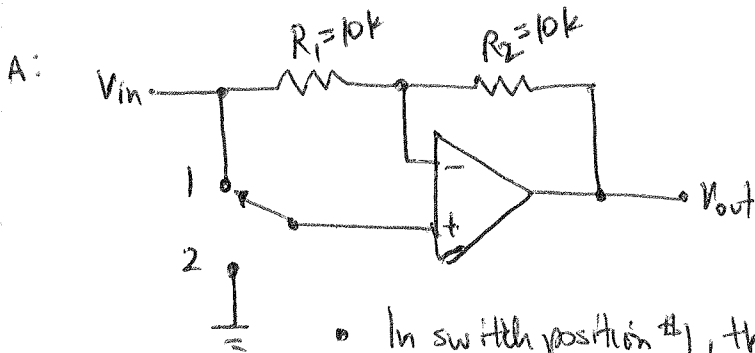4.3 Analyze the "optional^{*} inverter" circuits of Fig. 4.14.



 - In switch position #1, there is no voltage across the 1st resistor (since $V_+ = V_-$), so no current flows through it. Therefore no current flows through the second resistor either and $V_{out} = V_- = V_+ = V_{in} \Rightarrow$ unity gain follower.
- In switch position #2, we have an inverting amplifier (see Fig. 4.4) with gain $= -\frac{R_2}{R_1} = -1$.



In switch position #1, no current flows through R_3 (5.1k Ω) since no current flows into an op-amp input.


Therefore $V_+ = V_{in} = V_-$

No voltage appears across R_1 , so no current flows in R_1 or R_2 ... $V_{out} = V_- = V_+ = V_{in}$
 \Rightarrow unity gain follower.

In switch position #2, $V_+ = 0$, so we have our ordinary inverting amplifier ... (V_- is a virtual ground) with gain $= -\frac{R_2}{R_1} = -1$
 Note that some current flows through R_3 (5.1k Ω) to ground so the input resistance is the parallel combination of R_1 and R_3 .

Ch 4 Additional Exercise #2: Design a capacitively coupled, non-inverting audio amplifier using an op-amp with gain = 20 dB, $Z_{in} = 10k$, and the -3dB point at 20 Hz

See fig. 4.6 on p. 179

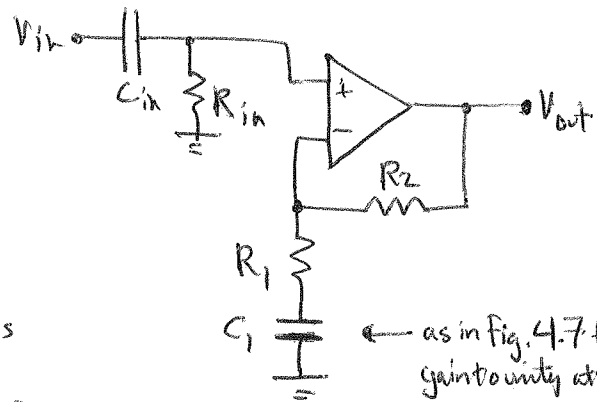

20 dB gain $\Rightarrow A_v = 10$
 on p. 178, we find

$A_v = 1 + \frac{R_2}{R_1}$ for this configuration so ... $\frac{R_2}{R_1} = 9$

... may choose $R_1 = 2.0k$ and $R_2 = 18k$ as in fig. 4.6


To get $Z_{in} = 10k$ in the passband ... choose $R_{in} = 10k$

To get $f_{3dB} = 20Hz$, choose C_{in} such that $\frac{1}{2\pi R_{in} C_{in}} = 20Hz$ or $C_{in} = 0.8 \mu F$

-5- and choose C_1 such that $\frac{1}{2\pi R_1 C_1} = 20Hz$ $C_1 = 4 \mu F$

 8.5

Use an exclusive-OR gate as an optional inverter



| A | B | Q |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

Use B as the control... if $B=0$ then...

| A | Q |
|---|---|
| 0 | 0 |
| 1 | 1 |

and the gate acts as a buffer without inversion

if $B=1$ then


| A | Q |
|---|---|
| 0 | 1 |
| 1 | 0 |

and the gate acts as an inverter.

8.7

What do the circuits in Fig. 8.12 do?

A:

 


NOR Gate Truth Table

| A | B | Q |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

| A | Q |
|---|---|
| 0 | 1 |
| 1 | 0 |

This is an inverter!

B:

 

AND Truth Table

| A | B | Q |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| A | Q |
|---|---|
| 0 | 0 |
| 1 | 1 |

This is a buffer!



NOR

| A | B | Q |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

→ BLOW

| A | Q |
|---|---|
| 0 | 1 |
| 1 | 0 |

This is also an inverter!




NOR

| A | B | Q |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 0 |

| B | Q |
|---|---|
| 0 | 0 |
| 1 | 0 |

Always returns a Low output.

 

AND

| A | B | Q |
|---|---|---|
| 0 | 0 | 0 |
| 0 | 1 | 0 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| A | Q |
|---|---|
| 0 | 0 |
| 1 | 0 |

Always returns a Low output.



NAND

| A | B | Q |
|---|---|---|
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

| B | Q |
|---|---|
| 0 | 1 |
| 1 | 0 |

This is an inverter.

8.8

Using 2-input gates show how to ~~use~~ make

(a) INVERT from NOR ... see 8.7 part A or part C



(b) OR from NORs ...

OR = NOT NOR so ...



(c) OR from NANDs ...

NAND $\Rightarrow \overline{A \bullet B} = \bar{A} + \bar{B}$ by DeMorgan's Theorem

or starting length $A + B = \overline{\overline{A + B}} = \overline{\bar{A} \bullet \bar{B}}$

A OR B = NOT (NOT A and NOT B)
 NAND (NOT A, NOT B)




Note that a NAND gate with both inputs connected together is an inverter



| NAND | | Q |
|------|---|---|
| A | B | |
| 0 | 0 | 1 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |


so ...

 

8.9

 (a) Make a 3-input AND gate from 2-input ANDs..


Note that $A \cdot B \cdot C = (A \cdot B) \cdot C = A \cdot (B \cdot C)$
 (see p. 491, table 8.3)



| A | B | C | Q |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

 (b) Make a 3-input OR gate from 2-input ORs

Note that $A + B + C = (A + B) + C = A + (B + C)$
 (see p. 491, table 8.3)



| A | B | C | Q |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 |

(c) Make a 3-input AND from 2-input NANDs

Since we can make INVERTERS out of NANDs...

